

# DE Question Bank

- 1) Realize a logic circuit for octal and binary encoder?
- 2) Implement a Full adder using 3x8 decoder?
- 3) Implement 3-Bit binary to gray code conversion
- 4) Design a priority encoder for a system with a 3 inputs
- 5) Design 7-segment decoder
- 6) What is magnitude comparator? Design 1-bit comparator and write the truth table, logic diagram using basic gates.
- 7) What is priority generator? Explain with an example.
- 8) What is Mux? Design 4 to 1 Mux using logic gates. write the truth table & explain it's working.
- 9) Construct 4:1 Mux using only 2:1 Mux.
- 10) Construct 8:1 Mux using only 2:1 Mux.
- 11) Design 16:1 Mux using 8:1 Mux & 2:1 Mux.
- 12) Realize  $Y = \overline{A}B + \overline{B}C + ABC$  using 8:1 Mux .
- 13) Implement using 4:1 Mux  $Y = f(A,B,C,D) = \sum m(0,1,2,4,6,9,12,14)$ .
- 14) Design and implement BCD to excess-3 code converter.
- 15) Explain working of Half Subtractor & Full Subtractor.
- 16) Realize working of 4-Bit Binary Parallel adder.
- 17) Design and implement Binary to gray code converter .
- 18)  $Y = f(a,b,c) = \sum m(0,1,6,7)$  realize following function by using 8:1nMux and 4:1 Mux.
- 19) Construct Full adder using only NAND gates.
- 20) Design BCD decimal decoder.
- 21) Construct Full adder using Half adder ,Construct the truth table.
- 22) Write the difference between flip flop & latch.
- 23) Write the difference between Sequential circuit and Combinational Circuit.
- 24) Write a circuit diagram , truth table , characteristics and Excitation table for i)SR flip flop ii)JK flip flop iii)D flip flop & iv) T flip flop.